

$$1. \quad V_b - V_d = \left[\frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2)(R_3 + R_4)} \right] V$$

$$= \left[\frac{600 - 200}{(30)(50)} \right] \times 15 = 4 \text{ volt}$$

2. Solve by symmetry

3. Let R_e is the effective resistance between a and b. The equivalent circuit is

$$\text{Now, } R_{ab} = R + \frac{R R_e}{R + R_e} \Rightarrow R_e = \frac{R^2 + 2R R_e}{R + R_e}$$

$$\Rightarrow R_e^2 - R R_e - R^2 = 0 \Rightarrow R_e = \left[\frac{\sqrt{5} + 1}{2} \right] R$$


$$R_e = \left[\frac{\sqrt{5} + 1}{2} \right] [1.235] = \left[\frac{\sqrt{5} + 1}{2} \right] [2.235 - 1]$$

$$= \left[\frac{\sqrt{5} + 1}{2} \right] [\sqrt{5} - 1] = \frac{4}{2} = 2\Omega$$

4. $R_{AB} = \frac{3R}{4}$

5. Ohm's law is TRUE, when the resistivity of the material is independent of the applied electric field.

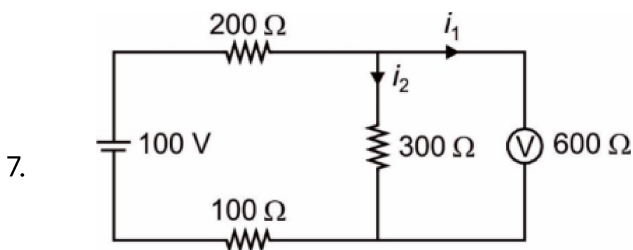6. Mobility, $\mu = \frac{V_d}{E} = \frac{\frac{J}{ne}}{\frac{J}{\sigma}} = \frac{\sigma}{ne} = \text{const.}$



$R_{eq} = 500$


$$i = \frac{100}{500} = \frac{1}{5} \text{ A} \Rightarrow i_2 = \frac{1}{5} \times \frac{600}{900} = \frac{6}{45} \text{ A}$$

$$V = \frac{6}{45} \times 300 = 40 \text{ V}$$

8. $V_d = \frac{-e \vec{E}_\tau}{m} \Rightarrow V_d \propto E$

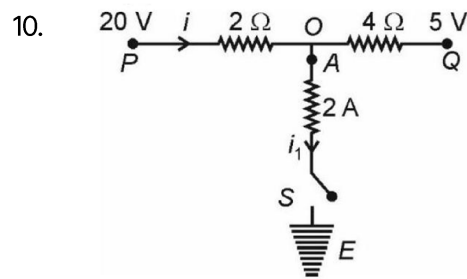9. $E = E_1 + E_2 = 6 \text{ V} \Rightarrow R_{eq} = 6\Omega \Rightarrow i = \frac{6}{6} = 1 \text{ A}$

Current through $6\Omega = \frac{1}{3} \text{ A}$



Apply K.V.L in POQ

$$20 - 2i - 4(i - i_1) = 5$$

$$6i - 4i_1 = 15$$

Apply K.V.L in POE

$$20 - 2i - 2i_1 = 0 \Rightarrow i + i_1 = 10$$


On solving (i) and (ii)

$$i_1 = 4.5 \text{ A}$$

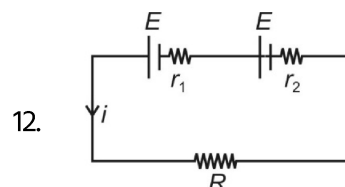11. No current flows via capacitor

$$V_c = V_{r_2}$$

$$V_c = \frac{E r_2}{r + r_2} \Rightarrow \frac{q}{C} = V_c \Rightarrow q = \frac{C E r_2}{r + r_2}$$




12.

$$V = E_1 - i r_1 = 0 \Rightarrow i = \frac{E}{r_1}$$

$$i = \frac{2E}{R+r_1+r_2} = \frac{E}{r_1}$$

$$R+r_1+r_2 = 2r_1 \Rightarrow R = r_1 - r_2$$

14.

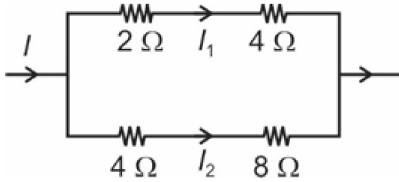

Power consumed by 8Ω resistance is 8 W

$$\therefore P = (I_2)^2 \times 8 = 8$$

$$\therefore I_2 = 1 \text{ A}$$

For parallel circuits $I_1(2+4) = I_2(4+8)$

$$I_1 = I_2 \times \frac{12}{6} = 1 \times 2 = 2 \text{ A}$$

Now current through 2Ω resistance is 2 A

$$P_2 = (I_1)^2 \times R = (2)^2 \times (2) = 8 \text{ W}$$


16.

$$i = \frac{\frac{20}{3} \times 1}{\frac{20}{3} + 60} \Rightarrow i = \frac{20}{200} = 0.1$$

17.

Aluminium is conductor and its resistivity increases with temperature but semiconductor Si has negative coefficient of resistivity. So as temperature increases, its resistivity decreases.

18.

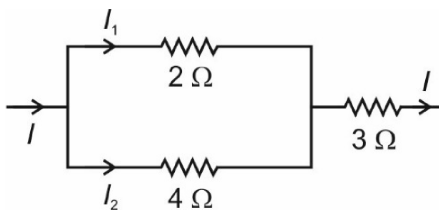

$$\text{Heat in } 2\Omega \text{ resistor } H_1 = (I_1)^2 \times 2 \times t$$

$$\text{Heat in } 4\Omega \text{ resistor } H_2 = (I_2)^2 \times 4 \times t$$

$$\text{Heat in } 3\Omega \text{ resistor } H_3 = (I)^2 \times 3 \times t$$

$$\text{But } I_1 = I \times \frac{4}{2+4} = \frac{2}{3}I \Rightarrow I_2 = I \times \frac{2}{2+4} = \frac{1}{3}I$$

$$\therefore H_1 : H_2 : H_3 :: \left(\frac{2}{3}I\right)^2 \times 2 \times t : \left(\frac{1}{3}I\right)^2$$

$$\times 4 \times t : (I)^2 \times 3 \times t$$


$$H_1 : H_2 : H_3 :: \frac{8}{9} : \frac{4}{9} : 3 \Rightarrow H_1 : H_2 : H_3 :: 8 : 4 : 27$$

19. $i = neAv = \frac{neA}{4}v_1 \Rightarrow v_1 = 4v$

20. $\frac{P_2}{P_1} = \left(\frac{V_2}{V_1}\right)^2 \Rightarrow P_2 = P_1 \left[\frac{V_2}{V_1}\right]^2$

$$= 1000 \left[\frac{50}{200}\right]^2 = 1000 \times \frac{1}{16} = 62.5 \text{ W}$$

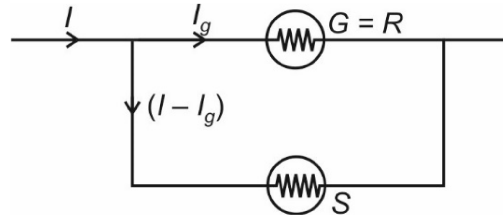
21. Required shunt = $\frac{\text{Original connected resistance}}{(\text{Range} - 1)}$



$$(I - I_g)S = I_g R \Rightarrow (nI_g - I_g)S = I_g R$$

$$(n-1)I_g S = I_g \times R \Rightarrow S = \frac{R}{n-1}$$


22.

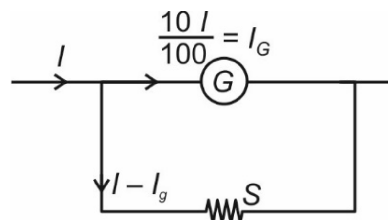

$$I_g \times G = (I - I_g) \times S$$

$$0.1 \times 99 = (0.9)I \times S$$

23.

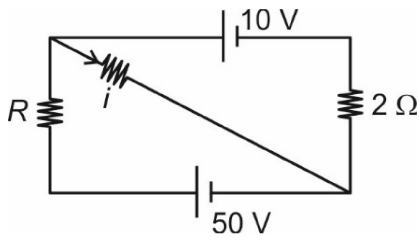

$$\text{For } i = 0 \Rightarrow \frac{10}{2} = \frac{50}{R}$$

$$24. v_d = \left(\frac{eE}{m}\right)\tau \Rightarrow v_d = \frac{e\tau}{m} \left(\frac{V}{l}\right) \propto \frac{1}{l}$$

$$l \rightarrow \frac{l}{2} \Rightarrow l \rightarrow \frac{l}{2}$$

25. Direction of magnetic force remains perpendicular to direction of velocity so no work is done on charge particle.

$$26. \frac{\mu_0 N I R^2}{2(R^2 + x^2)^{3/2}} = \frac{1}{8} \Rightarrow \therefore = \sqrt{3}R$$

$$\frac{\mu_0 N I}{2R}$$

27. Net force on current carrying loop in uniform magnetic field is zero.

28. Same? same momentum. $\left(\lambda = \frac{h}{p}\right)$

$$r = \frac{mv}{qB} \Rightarrow r \propto \frac{1}{q}$$


$$r_p : r_\alpha \equiv \frac{1}{q_p} : \frac{1}{q_\alpha} \Rightarrow q_\alpha = 2q_p = 2 : 1$$

$$29. \vec{\tau} = \vec{M} \times \vec{B} = 50 \hat{i} \times (0.5 \hat{i} + 3 \hat{j}) = 150 \text{ kNm}$$

$$30. r = \sqrt{x^2 + y^2} \Rightarrow \vec{B} = B \sin \theta \hat{i} - B \cos \theta \hat{j}$$

$$= \frac{\mu_0 I}{2\pi r} \left[\frac{y}{r} \hat{i} - \frac{x}{r} \hat{j} \right] = \frac{\mu_0 I}{2\pi r^2} (y \hat{i} - x \hat{j})$$
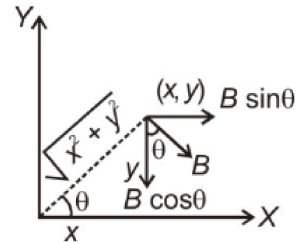
$$= \frac{\mu_0 I}{2\pi} \frac{(y \hat{i} - x \hat{j})}{(x^2 + y^2)}$$



31. Lorentz force

$$\vec{F} = q\vec{E} + q(\vec{v} \times \vec{B})$$

$\vec{F} = 0$, if particle was unaccelerated.

$$32. B = B_1 - B_2 = \frac{\mu_0 i}{24} \left(\frac{1}{a} - \frac{1}{b} \right) \Rightarrow B = \frac{\mu_0 i}{24} \left(\frac{b-a}{ab} \right)$$

$$33. \text{Radius of path } r = \frac{\sqrt{2Km}}{qB} \Rightarrow r \propto \sqrt{m}$$


Radius of proton path > Radius of electron path

$$\text{curvature} \propto \frac{1}{\text{Radius}}$$

$$34. F_m = I \vec{\ell} \times \vec{B} \Rightarrow I \ell (\hat{j} \times \hat{i} + 2\hat{j} \times \hat{j} + 2\hat{j} \times \hat{k}) B_0$$

$$I \ell B_0 (-\hat{k} + 2\hat{i}) = \sqrt{5} I \ell B_0$$

35.

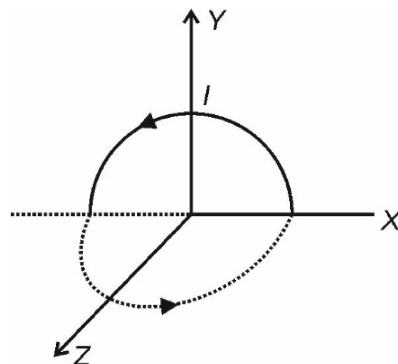

$$\vec{B} = \vec{B}_1 + \vec{B}_2 ; \vec{B} = \frac{\mu_0 I}{4R} \hat{j} + \frac{\mu_0 I}{4R} \hat{k} \Rightarrow |\vec{B}| = \frac{\mu_0 I}{2\sqrt{2}R}$$

36. $V = \text{constan}$


$$t \Rightarrow \& q\vec{E} = q(\vec{v} \times \vec{B}) \Rightarrow \& \vec{E} \perp \vec{B}$$

37. $2\pi r = L \Rightarrow M = IA = l \times \pi r^2$

$$= l \times \pi \times \left[\frac{L}{2\pi} \right]^2 = l \frac{L^2}{4\pi}$$

38. $B_1 = B_2 \Rightarrow \frac{\mu_0 i_1}{2r_1} = \frac{\mu_0 i_2}{2r_2} \Rightarrow \frac{i_1}{i_2} = \frac{r_1}{r_2} = \frac{1}{2}$

39. Force acting on conductor is like

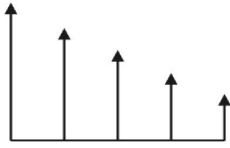

So, it will turn clockwise.

40. $= \frac{qEx^2}{2mv^2} \Rightarrow y = \frac{qEx^2}{4(qV)} \Rightarrow y = \frac{Ex^2}{4V}$

41. $B = 2 \left[\frac{\mu_0 I}{4\pi a} (\sin 45^\circ + \sin 90^\circ) \right]$


42. $B = \frac{\mu_0 I}{2R} = \frac{\mu_0 qf}{2R} = \frac{\mu_0 q\omega}{4\pi R}$

44. $B2\pi r = \frac{\mu_0 / r^2}{R^2} \Rightarrow \therefore B = \frac{\mu_0 I r}{2\pi R^2} = \frac{\mu_0 I}{8\pi}$

45. $\frac{T_1}{T_2} = \frac{m_1}{m_2} = \frac{1}{2} \left[\because T = \frac{2\pi m}{qB} \right] \Rightarrow \therefore \frac{K_1}{K_2} = \frac{m_1}{m_2} = \frac{1}{2}$

Answer-Key

1.	4	2.	4	3.	3	4.	4	5.	4	6.	4	7.	3	8.	4	9.	1	10.	1
11.	2	12.	3	13.	1	14.	2	15.	4	16.	1	17.	1	18.	2	19.	4	20.	1
21.	2	22.	2	23.	1	24.	1	25.	4	26.	3	27.	3	28.	4	29.	2	30.	1
31.	2	32.	2	33.	2	34.	1	35.	3	36.	2	37.	4	38.	4	39.	2	40.	2
41.	1	42.	2	43.	3	44.	3	45.	2	46.	1	47.	3	48.	2	49.	4	50.	3
51.	3	52.	4	53.	4	54.	1	55.	4	56.	1	57.	3	58.	4	59.	1	60.	2
61.	1	62.	3	63.	3	64.	4	65.	1	66.	4	67.	3	68.	2	69.	4	70.	2
71.	4	72.	2	73.	1	74.	2	75.	4	76.	2	77.	1	78.	2	79.	4	80.	3
81.	1	82.	3	83.	4	84.	4	85.	1	86.	4	87.	1	88.	1	89.	3	90.	4
91.	2	92.	2	93.	2	94.	1	95.	3	96.	3	97.	2	98.	2	99.	3	100.	2
101.	1	102.	2	103.	3	104.	3	105.	2	106.	2	107.	3	108.	4	109.	2	110.	3
111.	2	112.	2	113.	4	114.	3	115.	1	116.	3	117.	4	118.	2	119.	3	120.	2
121.	1	122.	3	123.	4	124.	2	125.	4	126.	3	127.	4	128.	3	129.	4	130.	3
131.	3	132.	2	133.	4	134.	3	135.	4	136.	3	137.	3	138.	3	139.	2	140.	2
141.	3	142.	3	143.	3	144.	2	145.	4	146.	1	147.	3	148.	1	149.	4	150.	1
151.	3	152.	2	153.	3	154.	2	155.	3	156.	2	157.	3	158.	3	159.	1	160.	1
161.	3	162.	3	163.	1	164.	1	165.	1	166.	1	167.	2	168.	2	169.	1	170.	4
171.	2	172.	3	173.	2	174.	1	175.	1	176.	2	177.	2	178.	3	179.	1	180.	3

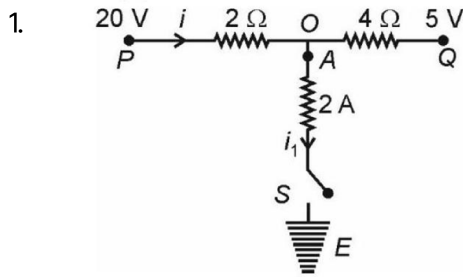

Apply K.V.L in POQ

$$20 - 2i - 4(i - i_1) = 5$$

$$6i - 4i_1 = 15$$

Apply K.V.L in POE

$$20 - 2i - 2i_1 = 0 \Rightarrow i + i_1 = 10$$

On solving (i) and (ii)


$$i_1 = 4.5A$$

2. No current flows via capacitor

$$V_c = V_{r_2}$$

$$V_c = \frac{Er_2}{r+r_2} \Rightarrow \frac{q}{C} = V_c \Rightarrow q = \frac{CEr_2}{r+r_2}$$

3.

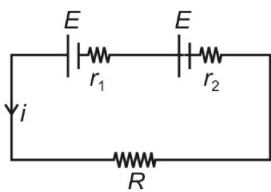


$$V = E_i - ir_1 = 0 \Rightarrow i = \frac{E}{r_1}; i = \frac{2E}{R+r_1+r_2} = \frac{E}{r_1}$$

$$R + r_1 + r_2 = 2r_1 \Rightarrow R = r_1 - r_2$$

4. Aluminium is conductor and its resistivity increases with temperature but semiconductor Si has negative coefficient of resistivity. So as temperature increases, its resistivity decreases.

5.

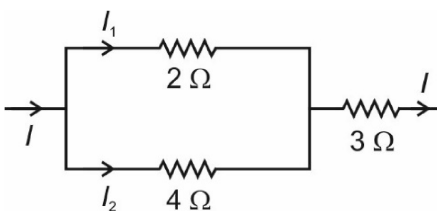

$$\text{Heat in } 2\Omega \text{ resistor } H_1 = (I_1)^2 \times 2 \times t$$

$$\text{Heat in } 4\Omega \text{ resistor } H_2 = (I_2)^2 \times 4 \times t$$

$$\text{Heat in } 3\Omega \text{ resistor } H_3 = (I)^2 \times 3 \times t$$

$$\text{But } I_1 = I \times \frac{4}{2+4} = \frac{2}{3}I \Rightarrow I_2 = I \times \frac{2}{2+4} = \frac{1}{3}I$$

$$\therefore H_1 : H_2 : H_3 :: \left(\frac{2}{3}I\right)^2 \times 2 \times t : \left(\frac{1}{3}I\right)^2$$

$$\times 4 \times t : (I)^2 \times 3 \times t$$

$$H_1 : H_2 : H_3 :: \frac{8}{9} : \frac{4}{9} : 3 \Rightarrow H_1 : H_2 : H_3 :: 8 : 4 : 27$$

6. $i = neAv = \frac{neA}{4} v_1 \Rightarrow v_1 = 4v$

7. Let R_e is the effective resistance between a and b. The equivalent circuit is

$$\text{Now, } R_{ab} = R + \frac{RR_e}{R+R_e} \Rightarrow R_e = \frac{R^2 + 2RR_e}{R+R_e}$$

$$\Rightarrow R_e^2 - RR_e - R^2 = 0 \Rightarrow R_e = \left[\frac{\sqrt{5}+1}{2} \right] R$$

$$R_e = \left[\frac{\sqrt{5}+1}{2} \right] [1.235] = \left[\frac{\sqrt{5}+1}{2} \right] [2.235 - 1]$$

$$= \left[\frac{\sqrt{5}+1}{2} \right] [\sqrt{5}-1] = \frac{4}{2} = 2\Omega$$

8. $R_{AB} = \frac{3R}{4}$

9. Ohm's law is TRUE, when the resistivity of the material is independent of the applied electric field.

10. $v_d = \left(\frac{eE}{m}\right) \tau \Rightarrow v_d = \frac{e\tau}{m} \left(\frac{V}{l}\right) \propto \frac{1}{l}$

$$l \rightarrow \frac{1}{2} \Rightarrow I \rightarrow \frac{1}{2}$$

11. Direction of magnetic force remains perpendicular to direction of velocity so no work is done on charge particle.

$$\frac{\mu_0 N I R^2}{2(R^2 + x^2)^{3/2}} = \frac{1}{8} \Rightarrow \therefore = \sqrt{3}R$$

13. Lorentz force

$$\vec{F} = q\vec{E} + q(\vec{v} \times \vec{B})$$

$$\vec{F} = 0, \text{ if particle was unaccelerated.}$$

14. $B = B_1 - B_2 = \frac{\mu_0 i}{24} \left(\frac{1}{a} - \frac{1}{b} \right) \Rightarrow B = \frac{\mu_0 i}{24} \left(\frac{b-a}{ab} \right)$


15. Radius of path $r = \frac{\sqrt{2Km}}{qB} \Rightarrow r \propto \sqrt{m}$

Radius of proton path > Radius of electron path

$$\text{curvature} \propto \frac{1}{\text{Radius}}$$


16. $B_1 = B_2 \Rightarrow \frac{\mu_0 i_1}{2r_1} = \frac{\mu_0 i_2}{2r_2} \Rightarrow \frac{i_1}{i_2} = \frac{r_1}{r_2} = \frac{1}{2}$

17. Force acting on conductor is like

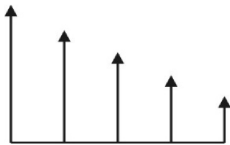

So, it will turn clockwise.

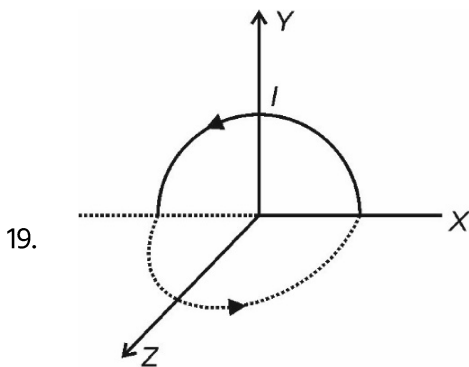18. $= \frac{qEx^2}{2mv^2} \Rightarrow y = \frac{qEx^2}{4(qV)} \Rightarrow y = \frac{Ex^2}{4V}$



$$\vec{B} = \vec{B}_1 + \vec{B}_2 ; \vec{B} = \frac{\mu_0 I}{4R} \hat{j} + \frac{\mu_0 I}{4R} \hat{k} \Rightarrow |\vec{B}| = \frac{\mu_0 I}{2\sqrt{2}R}$$

20. $V = \text{constan}$

$$t \Rightarrow \& q\vec{E} = q(\vec{v} \times \vec{B}) \Rightarrow \& \vec{E} \perp \vec{B}$$

21. $2\pi r = L \Rightarrow M = IA = I \times \pi r^2$

$$= I \times \pi \times \left[\frac{L}{2\pi} \right]^2 = I \frac{L^2}{4\pi}$$

22. $B = 2 \left[\frac{\mu_0 I}{4\pi a} (\sin 45^\circ + \sin 90^\circ) \right]$

23. $B = \frac{\mu_0 I}{2R} = \frac{\mu_0 qf}{2R} = \frac{\mu_0 q\omega}{4\pi R}$

25. Net force on current carrying loop in uniform magnetic field is zero.

26. Same? same momentum. $\left(\lambda = \frac{h}{p} \right)$

$$r = \frac{mv}{qB} \Rightarrow r \propto \frac{1}{q}$$


$$r_p : r_\alpha \equiv \frac{1}{q_p} : \frac{1}{q_\alpha} \Rightarrow q_\alpha = 2q_p = 2 : 1$$

27. $\vec{\tau} = \vec{M} \times \vec{B} = 50 \hat{i} \times (0.5 \hat{i} + 3 \hat{j}) = 150 \text{ kNm}$

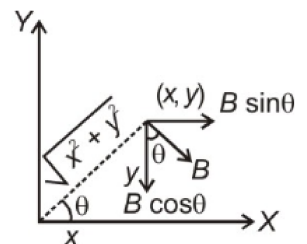28. $r = \sqrt{x^2 + y^2} \Rightarrow \vec{B} = B \sin \theta \hat{i} - B \cos \theta \hat{j}$


$$= \frac{\mu_0 I}{2\pi r} \left[\frac{y}{r} \hat{i} - \frac{x}{r} \hat{j} \right] = \frac{\mu_0 I}{2\pi r^2} (y \hat{i} - x \hat{j})$$

$$= \frac{\mu_0 I}{2\pi} \frac{(y \hat{i} - x \hat{j})}{(x^2 + y^2)}$$




29. $\frac{P_2}{P_1} = \left(\frac{V_2}{V_1}\right)^2 \Rightarrow P_2 = P_1 \left[\frac{V_2}{V_1}\right]^2$
 $= 1000 \left[\frac{50}{200}\right]^2 = 1000 \times \frac{1}{16} = 62.5W$

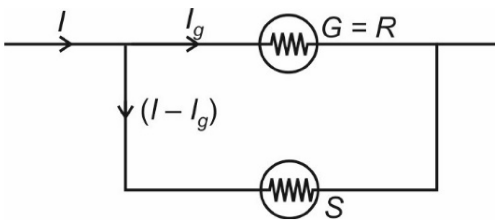30. Required shunt = $\frac{\text{Original connected resistance}}{(\text{Range} - 1)}$




$(I - I_g)S = I_g G \Rightarrow (nI_g - I_g)S = I_g R$

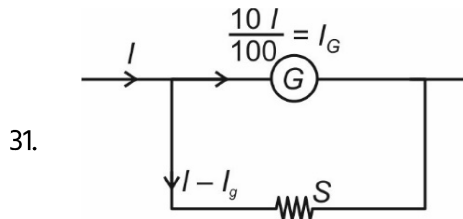$(n-1)I_g S = I_g \times R \Rightarrow S = \frac{R}{n-1}$



$I_g \times G = (I - I_g) \times S$

$0.1 \times 99 = (0.9)I \times S$

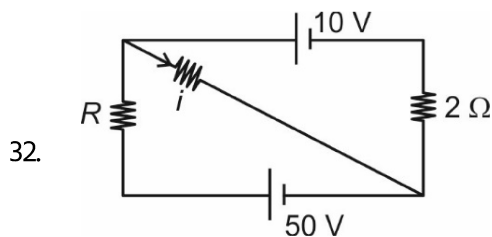

For $i = 0 \Rightarrow \frac{10}{2} = \frac{50}{R}$


33. $F_m = I \vec{\ell} \times \vec{B} \Rightarrow I \ell (\hat{j} \times \hat{i} + 2\hat{j} \times \hat{j} + 2\hat{j} \times \hat{k}) B_0$

$I \ell B_0 (-\hat{k} + 2\hat{i}) = \sqrt{5} I \ell B_0$

34. $B 2\pi r = \frac{\mu_0 I}{R^2}$

$\therefore B = \frac{\mu_0 I r}{2\pi R^2} = \frac{\mu_0 I}{8\pi}$

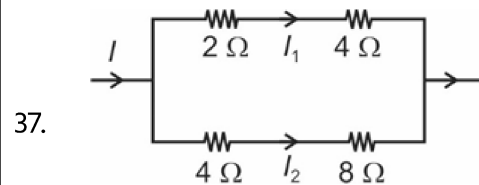35. $\frac{T_1}{T_2} = \frac{m_1}{m_2} = \frac{1}{2} \left[\because T = \frac{2\pi m}{qB} \right] \Rightarrow \therefore \frac{K_1}{K_2} = \frac{m_1}{m_2} = \frac{1}{2}$



Power consumed by 8Ω resistance is 8 W

$\therefore P = (I_2)^2 \times 8 = 8$

$\therefore I_2 = 1 A$

For parallel circuits $I_1(2 + 4) = I_2(4 + 8)$


$I_1 = I_2 \times \frac{12}{6} = 1 \times 2 = 2 A$

Now current through 2Ω resistance is 2 A

$P_2 = (I_1)^2 \times R = (2)^2 \times (2) = 8 W$

39. $i = \frac{\frac{20}{3} \times 1}{\frac{20}{3} + 60} \Rightarrow i = \frac{20}{200} = 0.1$

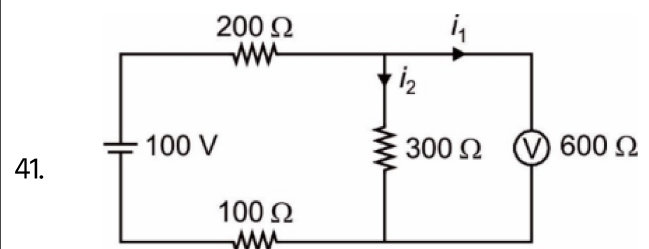40. Mobility, $\mu = \frac{V_d}{E} = \frac{\frac{J}{ne}}{\frac{J}{\sigma}} = \frac{\sigma}{ne} = \text{const.}$



$$R_{eq} = 500$$

$$i = \frac{100}{500} = \frac{1}{5} \text{ A} \Rightarrow i_2 = \frac{1}{5} \times \frac{600}{900} = \frac{6}{45} \text{ A}$$

$$V = \frac{6}{45} \times 300 = 40 \text{ V}$$

42. $V_d = \frac{-e\vec{E}_\tau}{m} \Rightarrow V_d \propto E$

43. $E = E_1 + E_2 = 6 \text{ V} \Rightarrow R_{eq} = 6\Omega \Rightarrow i = \frac{6}{6} = 1 \text{ A}$

Current through $6\Omega = \frac{1}{3} \text{ A}$

44. $V_b - V_d = \left[\frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2)(R_3 + R_4)} \right] V$
 $= \left[\frac{600 - 200}{(30)(50)} \right] \times 15 = 4 \text{ volt}$

45. Solve by symmetry

Answer-Key

1.	1	2.	2	3.	3	4.	1	5.	2	6.	4	7.	3	8.	4	9.	4	10.	1
11.	4	12.	3	13.	2	14.	2	15.	2	16.	4	17.	2	18.	2	19.	3	20.	2
21.	4	22.	1	23.	2	24.	3	25.	3	26.	4	27.	2	28.	1	29.	1	30.	2
31.	2	32.	1	33.	1	34.	3	35.	2	36.	1	37.	2	38.	4	39.	1	40.	4
41.	3	42.	4	43.	1	44.	4	45.	4	46.	4	47.	1	48.	4	49.	3	50.	4
51.	1	52.	2	53.	4	54.	2	55.	1	56.	3	57.	1	58.	3	59.	4	60.	1
61.	1	62.	4	63.	4	64.	1	65.	1	66.	2	67.	4	68.	4	69.	3	70.	2
71.	3	72.	4	73.	1	74.	3	75.	3	76.	4	77.	2	78.	1	79.	3	80.	3
81.	4	82.	2	83.	4	84.	2	85.	4	86.	1	87.	1	88.	3	89.	2	90.	4
91.	2	92.	1	93.	2	94.	2	95.	3	96.	4	97.	2	98.	4	99.	3	100.	2
101.	3	102.	2	103.	4	104.	3	105.	4	106.	4	107.	3	108.	4	109.	1	110.	3
111.	3	112.	2	113.	2	114.	2	115.	2	116.	4	117.	3	118.	3	119.	3	120.	2
121.	1	122.	3	123.	4	124.	1	125.	3	126.	4	127.	2	128.	3	129.	2	130.	3
131.	3	132.	2	133.	2	134.	2	135.	3	136.	1	137.	3	138.	1	139.	3	140.	2
141.	3	142.	1	143.	1	144.	1	145.	2	146.	1	147.	1	148.	2	149.	2	150.	3
151.	2	152.	3	153.	2	154.	3	155.	3	156.	1	157.	4	158.	2	159.	3	160.	3
161.	1	162.	3	163.	2	164.	2	165.	2	166.	2	167.	1	168.	3	169.	1	170.	1
171.	4	172.	1	173.	3	174.	3	175.	3	176.	2	177.	4	178.	3	179.	3	180.	3